

Budapest University of Technology and Economics

Faculty of Natural Sciences

M3 - Study of Comparators

Lab report

04/11/2026

Lab responsible
Viktor Farkas

Student
Abigél ORTUTAY (UGHRKC)
Physics-engineering BSc 3rd year
abico.ortutay@gmail.com

Student
Hanna ERTL (SPH4U7)
Physics-engineering BSc 3rd year
hannavedaertl@gmail.com

Abstract

1 Theoretical introduction

2 Measurement tools

For this measurement, we used the following list of tools:

- ST μA741CN operational amplifier
- TI TL071CP operational amplifier
- OK Industries Inc. CM-140 L breadboard
- Resistors: 22 kΩ (1 piece), 10 kΩ (2 pieces), 100 kΩ (1 piece), 1 kΩ (1 piece)
- Jumping wires (6 pieces)
- Crocodile clips (6 pieces)
- Banana plugs (6 pieces)
- Capacitor: 6.8 nF (1 piece)
- HM8040-2 HAMEG Triple power supply
- HM 8011-3 HAMEG Digital multimeter
- SIGLENT SDS 1072CML Digital storage oscilloscope
- Handheld multimeter

3 Measurement setup

4 Measurements

4.1 Switching voltage of the comparator with an operational amplifier

For the first measurement, we had the ciruit setup as seen on figure 1 and described in the Measurement Setup section above.

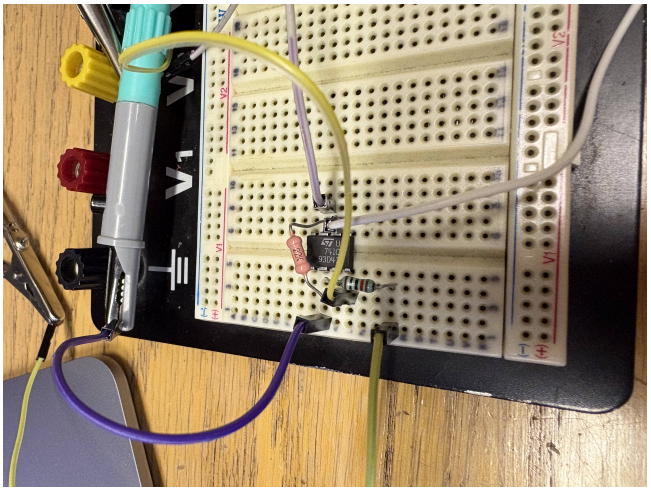


Figure 1: Simple comparator setup with two resistors

We wanted to determine the switching threshold of the configuration. We began varying the the voltage, satrting from 5V on the input, we found the output to be 4.468V. At this voltage we expected the output to be saturated to the positive supply value, which is mostly what we found, with a deviation of value:

$$Deviation = \frac{U_{+supp} - U_{out}}{U_{+supp}} = \frac{5 - 4.468}{5} = 0.106$$

As the configuration acts as a voltage divider on the non-inverting input of the operational amplifier, from this we could calculate that we suspect the switching threshold to be around:

$$U_+ = \frac{R_2}{R_1 + R_2} \cdot U_{+supp} = \frac{10}{32} \cdot 5 = 1.5625V$$

Varying the voltage, experimentally we found the switching threshold to be at 1.6 V, where the output showed -3.058 V on the multimeter.
While the measured switching voltage is close to the theoretical value we expected at only 2.4% deviation, we expected the output to saturate to the negative supply at -5 V. However, we found that the output went no lower than -3.058 V.
We believe this could be because the operational amplifiers we used were not rail-to-rail devies. In this case the internal structure of the amplifier is such that voltage drops occur on the internal output stage transistors. The asymmetry of the voltage drops in the positive and negative saturation regimes can be due to the asymmetric output stage on which this voltage

drop occurs.
The difference we found between the magnitude of the output voltages on the two regimes was close to 4.468 - 3.058 = 1.41 V.

4.2 New switching voltage in Schmitt-trigger with operational amplifier

Altering the setup of the previous task by adding a resistor of 100 kΩ, we created the Schmitt-trigger setup. We expected the switching threshold to extend to an interval, as the purpose of the Schmitt-trigger setup was to reduce the sensitivity to input noise. We calculated the theoretical switching thresholds to be at:

$$U_1 = \frac{5}{1 + \frac{R_1}{R_2} + \frac{R_1}{R_3}} + \frac{U_{\text{out}}}{1 + \frac{R_3}{R_2} + \frac{R_3}{R_1}} = \frac{5\text{ V}}{1 + 2.2 + 0.22} + \frac{U_{\text{out}}}{1 + 10 + 4.545} = 1.462\text{ V} + \frac{U_{\text{out}}}{15.545}$$

$$U_{1+} = 1.462\text{ V} + \frac{5\text{ V}}{15.545} = 1.462\text{ V} + 0.322\text{ V} = 1.78\text{ V}$$

$$U_{1-} = 1.462\text{ V} + \frac{-5\text{ V}}{15.545} = 1.462\text{ V} - 0.322\text{ V} = 1.14\text{ V}$$

The measured switching thresholds were at 1.8 V and 1.3 V, at these thresholds the output switched to -3.086 V and 4.36 V respectively. The higher threshold - below which the output voltage saturates to the negative supply voltage - is very close to the theoretical value, with only 1% deviation. The lower threshold - where the output saturated to the positive supply voltage - deviated by 14%. We believe this signification deviation could also be a result of the resolution of the measurement device used. We could only be precise to 1 decimal point, at which point the deviation could have also been 9% at 1.25 V on the input, rounded up to 1.3 V.
The difference between the output voltage magnitudes stayed relatively unchanged, compared to the previous task.

4.3 Waveforms of the relaxation oscillator with operational amplifier

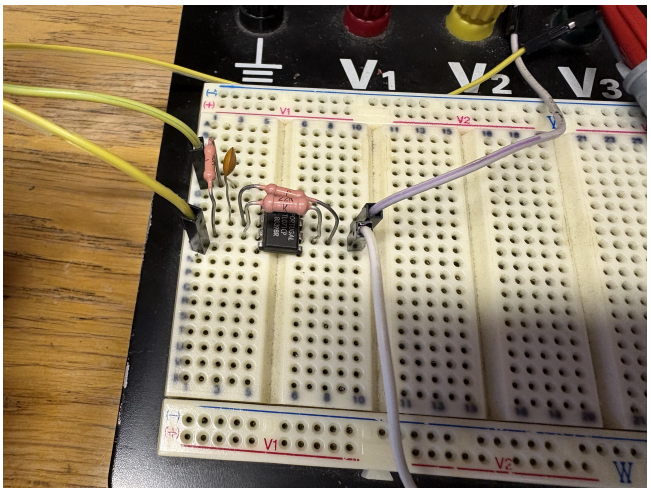


Figure 2: Relaxation oscillator setup with three resistors and one capacitor

To determine the value of the capacitance we needed to use in the relaxed oscillator setup, we used the following equations first to find the switching voltages, and then to determine the capacitance through the period equation knowing that the period is the inverse of the frequency:

$$U_{1s1} = U_+ \cdot \frac{R_2}{R_2 + R_3} \quad \text{and} \quad U_{1s2} = U_- \cdot \frac{R_2}{R_2 + R_3}$$


$$T = 2 \cdot R_1 \cdot C \cdot \ln\left(\frac{U_+ + U_{1s1}}{U_+ + U_{1s2}}\right)$$

$$C = \frac{1}{2 \cdot f \cdot R_1 \cdot \ln\left(1 + \frac{2R_2}{R_3}\right)} = 6.49 \text{ nF}$$


The capacitor with the closes value we found was that of 6.8 nF. Beginning with the TL071CP operational amplifier (seen in figure 3a, b, and c) we checked the waveform shapes of inputs and outputs, then we repeated this with the μA741CN operational amplifier (figure 3d, e, f). The observed shapes of the waveforms are summarised in the table below:

Operational Amplifier	U1	U2	Uo
TL071CP	Square	Triangle	Square
μA741CN	Trapeze	Soft triangle	Trapeze


Table 1: Observed waveforms of the noninverting (U1), inverting (U2), and output (Uo) signals with TL071CP and μA741CN operational amplifiers.

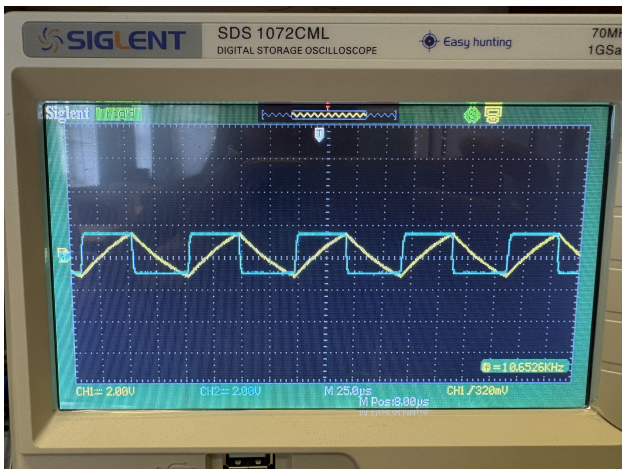

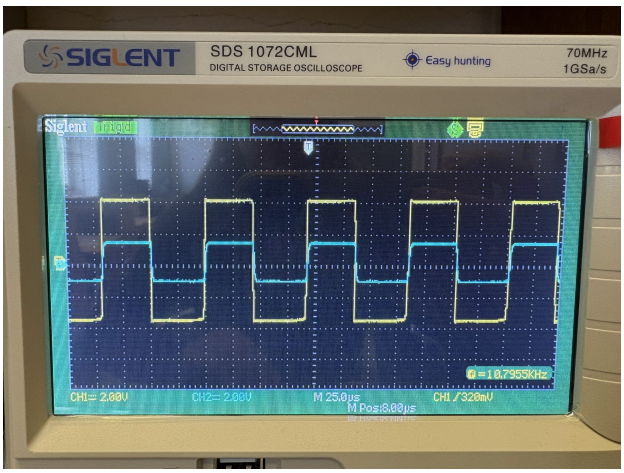
(a) TL: Measurement of U_1 on channel 2 and U_2 on channel 1



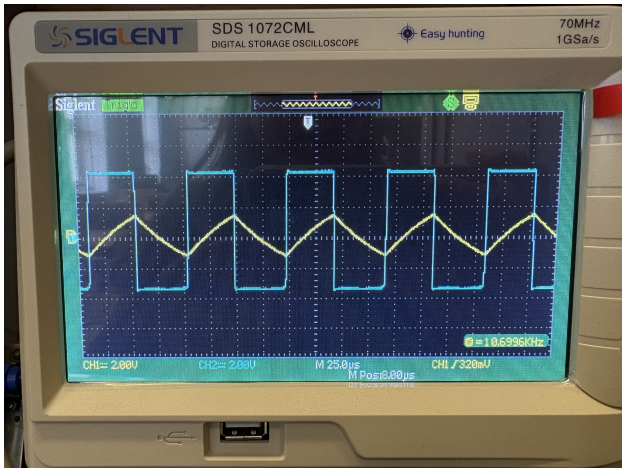
(b) TL: Measurement of U_1 on channel 2 and U_{out} on channel 1



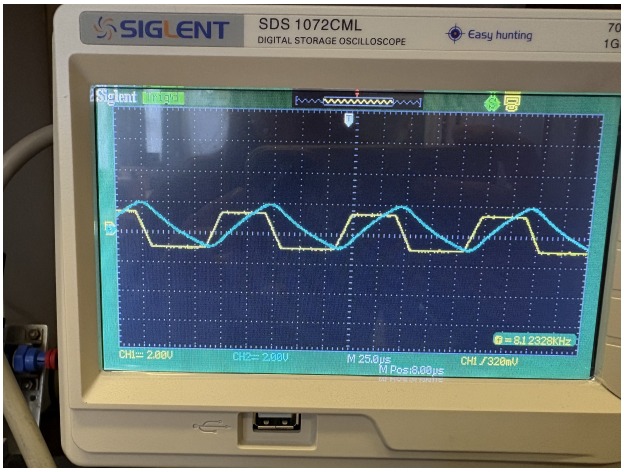
(c) TL: Measurement of U_{out} on channel 2 and U_2 on channel 1



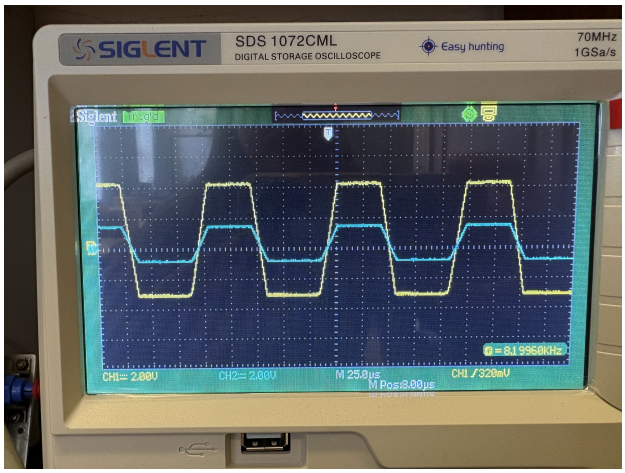(d) AU: Measurement of U_2 on channel 2 and U_1 on channel 1



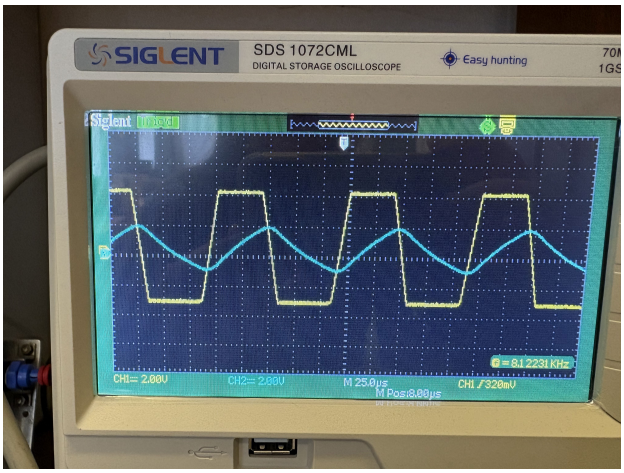(e) AU: Measurement of U_1 on channel 2 and U_{out} on channel 1



(f) AU: Measurement of U_2 on channel 2 and U_{out} on channel 1

Figure 3: Different measured waveforms of the relaxation oscillator setup with two operational amiplifiers, TL071CP and μA741CN; displaying inputs and output on the channels.

As seen in Table 1 and Figure 3, U1 and Uo share the same waveform shape with different

amplitude while U2 has a differing shape. When using TL U1 and Uo have ideal square waveform with steep edges showing fast switching, while U2 has an equally ideal triangle form with well defined peaks.
However, when using AU these shapes get rounded and distorted, the rising regime of the triangular waveform of both U1 and Uo are no longer as fast, while the triangle waveform of U2 turns into a rounded series of crests and troughs.
U1 and Uo have a similar shape as they are a result of a purely resistive voltage divider. On the other hand, U2 is governed by the RC constant, resulting in a charge and discharge behaviour which can be seen in the triangular form of the signal. In the case of the AU opamp, the low slew rate (SR = 0.5 V/μs) of the opamp causes the distortion of the waveforms, as it inhibits the instant switching we saw with the TL opamp having a much higher slew rate (SR = 13 V/μs).

4.4 Switching thresholds of the transistor Schmitt trigger circuit

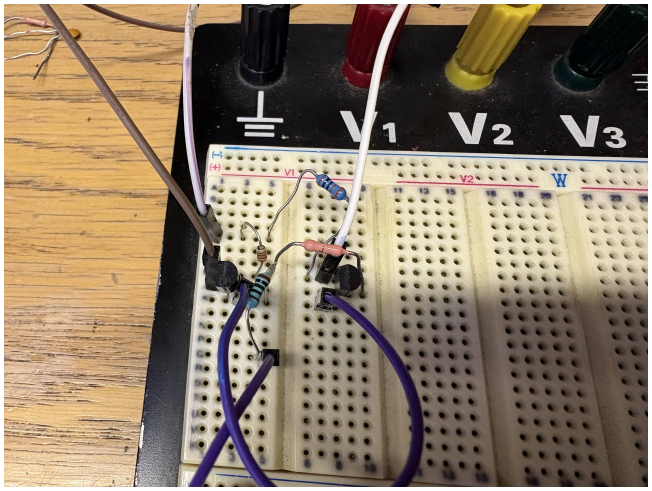


Figure 4: Schmitt trigger circuit setup with two transistors and four resistors

We configured the transistor Schmitt-trigger circuit, and measured the input switching thresholds of this configuration. We identified the input switching voltages to be around 1.2 - 1.3 V and 0.8 V, where we have 5.004 V and 0.523 V respectively. Between 0 and 1.2 V we observed a constant 0.523 V, which started rising to 0.69 V right before switching at 1.3 V. Similarly, we observed the 5.004 V decreasing. Using the following equations, the theoretical switching thresholds are:

$$U_{\text{in}\downarrow} = U_{E1} + U_{BE1} \approx 0.21 \text{ V} + 0.60 \text{ V} \approx 0.81 \text{ V}$$

$$U_{\text{in}\uparrow} = U_{E} + U_{BE1} \approx 0.55 \text{ V} + 0.65 \text{ V} \approx 1.20 \text{ V}$$

These theoretical values align with out measured values near perfectly, with 1% deviation error.

In the 0 - 1.2 V regime, T1 is off and T2 is on, this results in the output voltage being dictated by the saturation collector-emitter voltage of T2. Theoretically, the output voltage here is 0.54 V, given by the sum of the voltage drop on the shared emitter resistor and the saturation voltage of the collector-emitter on T2. Here we measured 0.523 V, giving only 3% error. As T1 starts to conduct the output voltage raises, this is what we measured between 1.2 - 1.3 V right before switching, where the output voltage was 0.69 V.
In the upper saturation limit, the output voltage should be the full 5 V of the positive supply theoretically, as T2 shuts off and T1 is saturated, delivering rail to rail output. However, here we measure a value 0.004 V above the positive supply voltage, we suspect this to be some inaccuracy of measurement, as it cannot be higher than the supply voltage, as energy cannot be created.
From these switching thresholds we calculate the experimental hysteresis - using the middle value of 1.2 - 1.3 V - to be 1.25 - 0.8 = 0.45 V. From the theoretical switching voltages (of 1.2 - 0.81) we get the theoretical hysteresis to be 0.39 V. Giving us a deviation of near 15% from the theoretical hysteresis. We believe this is also a result of the resolution of our triple supply device, as we were unable to set an input more precise than 1.2 or 1.3 V, it is possible that our switching threshold was closer to 1.2 V which would have resulted in only 2% deviation from the theoretical value.

5 Conclusion